What is Computation? Boolean Circuits and Finite State Machines

Carlotta Pavese

10.17.13

Carlotta Pavese What is Computation?

▲□→ < □→</p>

- ∢ ≣ ▶

Outline

What Can a Boolean Circuit Do?

Finite State Machines

Carlotta Pavese What is Computation?

・ロン ・四 と ・ ヨ と ・ ヨ と

Review

Computation and Functionalism

Functionalist understanding of minds: what they do

・ロト ・回ト ・ヨト ・ヨト

Review

Computation and Functionalism

- Functionalist understanding of minds: what they do
 - Abstracts from materials used to do those things

æ

Review

- Functionalist understanding of minds: what they do
 - Abstracts from materials used to do those things
- Computer science offers an account of computation that has exactly that abstract character

Review

- Functionalist understanding of minds: what they do
 - Abstracts from materials used to do those things
- Computer science offers an account of computation that has exactly that abstract character
- This parallel is not an accident!

Review

- Functionalist understanding of minds: what they do
 - Abstracts from materials used to do those things
- Computer science offers an account of computation that has exactly that abstract character
- This parallel is not an accident!
 - Putnam had computation in mind when he was advocating for functionalism!

Review

- Functionalist understanding of minds: what they do
 - Abstracts from materials used to do those things
- Computer science offers an account of computation that has exactly that abstract character
- This parallel is not an accident!
 - Putnam had computation in mind when he was advocating for functionalism!

Review

Computation and Functionalism

- Functionalist understanding of minds: what they do
 - Abstracts from materials used to do those things
- Computer science offers an account of computation that has exactly that abstract character
- This parallel is not an accident!
 - Putnam had computation in mind when he was advocating for functionalism!

Our Big Question

So what exactly is computation and are all mental activities just computation?

Today's Lecture Part 1: Boolean Circuits

Our Big Question

So what exactly is computation and are all mental activities just computation?

A ►

Today's Lecture Part 1: Boolean Circuits

Our Big Question

So what exactly is computation and are all mental activities just computation?

• First essential building block of computers:

Today's Lecture Part 1: Boolean Circuits

Our Big Question

So what exactly is computation and are all mental activities just computation?

- First essential building block of computers:
 - Boolean Circuits

Today's Lecture Part 1: Boolean Circuits

Our Big Question

So what exactly is computation and are all mental activities just computation?

- First essential building block of computers:
 - Boolean Circuits

Part of the Big Question

Today's Lecture Part 1: Boolean Circuits

Our Big Question

So what exactly is computation and are all mental activities just computation?

- First essential building block of computers:
 - Boolean Circuits
- Part of the Big Question
 - What exactly are Boolean circuits capable of?

Today's Lecture Part 1: Boolean Circuits

Our Big Question

So what exactly is computation and are all mental activities just computation?

- First essential building block of computers:
 - Boolean Circuits

Part of the Big Question

- What exactly are Boolean circuits capable of?
- Which mental activities can they perform?

Today's Lecture Part 1: Boolean Circuits

Our Big Question

So what exactly is computation and are all mental activities just computation?

- First essential building block of computers:
 - Boolean Circuits

Part of the Big Question

- What exactly are Boolean circuits capable of?
- Which mental activities can they perform?
- Which mental activities can't they perform?

Today's Lecture Part 2: Finite State Machines

Our Big Question

So what exactly is computation and are all mental activities just computation?

Today's Lecture Part 2: Finite State Machines

Our Big Question

So what exactly is computation and are all mental activities just computation?

Second essential building block of computers:

Today's Lecture Part 2: Finite State Machines

Our Big Question

So what exactly is computation and are all mental activities just computation?

- Second essential building block of computers:
 - Finite State Machine (FSM)

Today's Lecture Part 2: Finite State Machines

Our Big Question

So what exactly is computation and are all mental activities just computation?

- Second essential building block of computers:
 - Finite State Machine (FSM)

Part of the Big Question

Today's Lecture Part 2: Finite State Machines

Our Big Question

So what exactly is computation and are all mental activities just computation?

- Second essential building block of computers:
 - Finite State Machine (FSM)

Part of the Big Question

What exactly are FSMs capable of?

Today's Lecture Part 2: Finite State Machines

Our Big Question

So what exactly is computation and are all mental activities just computation?

- Second essential building block of computers:
 - Finite State Machine (FSM)

Part of the Big Question

- What exactly are FSMs capable of?
- Which mental activities can they perform?

Today's Lecture Part 2: Finite State Machines

Our Big Question

So what exactly is computation and are all mental activities just computation?

- Second essential building block of computers:
 - Finite State Machine (FSM)

Part of the Big Question

- What exactly are FSMs capable of?
- Which mental activities can they perform?
- Which mental activities can't they perform?

Preview Today's Class

1. When it comes to 'crunching bits', Boolean Circuits can do anything!

イロト イヨト イヨト イヨト

Preview Today's Class

- 1. When it comes to 'crunching bits', Boolean Circuits can do anything!
- 2. Some basic tasks require more than crunching bits and Boolean Circuits can't do them

A (1) > (1) > (1)

- 1. When it comes to 'crunching bits', Boolean Circuits can do anything!
- 2. Some basic tasks require more than crunching bits and Boolean Circuits can't do them
- 3. Minds can perform these tasks, so we must search on

- 1. When it comes to 'crunching bits', Boolean Circuits can do anything!
- 2. Some basic tasks require more than crunching bits and Boolean Circuits can't do them
- 3. Minds can perform these tasks, so we must search on
- 4. Finite State Machines can perform these tasks

- 1. When it comes to 'crunching bits', Boolean Circuits can do anything!
- 2. Some basic tasks require more than crunching bits and Boolean Circuits can't do them
- 3. Minds can perform these tasks, so we must search on
- 4. Finite State Machines can perform these tasks
 - They have a new component: a register

- 1. When it comes to 'crunching bits', Boolean Circuits can do anything!
- 2. Some basic tasks require more than crunching bits and Boolean Circuits can't do them
- 3. Minds can perform these tasks, so we must search on
- 4. Finite State Machines can perform these tasks
 - They have a new component: a register
- 5. We'll find things minds can do that FSMs can't

- 1. When it comes to 'crunching bits', Boolean Circuits can do anything!
- 2. Some basic tasks require more than crunching bits and Boolean Circuits can't do them
- 3. Minds can perform these tasks, so we must search on
- 4. Finite State Machines can perform these tasks
 - They have a new component: a register
- 5. We'll find things minds can do that FSMs can't
- 6. Computers consist of Boolean Circuits, an FSM and another component we'll discuss next week

Outline

What Can a Boolean Circuit Do?

Finite State Machines

Carlotta Pavese What is Computation?

<ロ> <同> <同> < 同> < 同> < 同> :

Boolean Logic

The Basics

• Algebra:
$$(x + y) + z = x + (y + z)$$

◆□→ ◆□→ ◆三→ ◆三→

Boolean Logic

The Basics

• Algebra:
$$(x + y) + z = x + (y + z)$$

Variables x, y, z can be any number

・ロン ・四と ・ヨン ・ヨン

Boolean Logic

The Basics

- Algebra: (x + y) + z = x + (y + z)
 - Variables x, y, z can be any number
 - $+, \times, -$, etc. operate on numbers

- 4 回 2 - 4 □ 2 - 4 □

Boolean Logic

The Basics

- Algebra: (x + y) + z = x + (y + z)
 - Variables x, y, z can be any number
 - ► +, ×, −, etc. operate on numbers
 - There are rules for correct calculation

|田・ (日) (日)

Boolean Logic

The Basics

- Algebra: (x + y) + z = x + (y + z)
 - ► Variables *x*, *y*, *z* can be any number
 - $+, \times, -$, etc. operate on numbers
 - There are rules for correct calculation
- Boolean Logic: $(A \land B) \land C = A \land (B \land C)$

個 ト く ヨ ト く ヨ ト
Boolean Logic

The Basics

- Algebra: (x + y) + z = x + (y + z)
 - ► Variables *x*, *y*, *z* can be any number
 - ► +,×, -, etc. operate on numbers
 - There are rules for correct calculation
- Boolean Logic: $(A \land B) \land C = A \land (B \land C)$
 - ► Variables A, B, C can be any true/false claim

向下 イヨト イヨト

Boolean Logic

The Basics

- Algebra: (x + y) + z = x + (y + z)
 - Variables x, y, z can be any number
 - ► +,×, -, etc. operate on numbers
 - There are rules for correct calculation
- Boolean Logic: $(A \land B) \land C = A \land (B \land C)$
 - Variables A, B, C can be any true/false claim
 - E.g. A can be: Obama ate yesterday

伺下 イヨト イヨト

Boolean Logic

The Basics

- Algebra: (x + y) + z = x + (y + z)
 - Variables x, y, z can be any number
 - ► +,×, -, etc. operate on numbers
 - There are rules for correct calculation
- Boolean Logic: $(A \land B) \land C = A \land (B \land C)$
 - ► Variables A, B, C can be any true/false claim
 - E.g. A can be: Obama ate yesterday
 - \land, \lor, \neg operate on truth/falsity of claims

▲圖 ▶ ▲ 臣 ▶ ▲ 臣 ▶

Boolean Logic

The Basics

- Algebra: (x + y) + z = x + (y + z)
 - Variables x, y, z can be any number
 - ► +,×, -, etc. operate on numbers
 - There are rules for correct calculation
- Boolean Logic: $(A \land B) \land C = A \land (B \land C)$
 - Variables A, B, C can be any true/false claim
 - E.g. A can be: Obama ate yesterday
 - \land, \lor, \neg operate on truth/falsity of claims
 - Just as and, or and not combine statements

・ 同 ト ・ 三 ト ・ 三 ト

Boolean Logic

The Basics

- Algebra: (x + y) + z = x + (y + z)
 - Variables x, y, z can be any number
 - ► +,×, -, etc. operate on numbers
 - There are rules for correct calculation
- Boolean Logic: $(A \land B) \land C = A \land (B \land C)$
 - Variables A, B, C can be any true/false claim
 - E.g. A can be: Obama ate yesterday
 - \land, \lor, \neg operate on truth/falsity of claims
 - Just as and, or and not combine statements
 - The way they operate give rise to certain laws

▲圖 ▶ ▲ 臣 ▶ ▲ 臣 ▶

Boolean Logic

The Basics

- Algebra: (x + y) + z = x + (y + z)
 - Variables x, y, z can be any number
 - ► +,×, -, etc. operate on numbers
 - There are rules for correct calculation
- ▶ Boolean Logic: $(A \land B) \land C = A \land (B \land C)$
 - Variables A, B, C can be any true/false claim
 - E.g. A can be: Obama ate yesterday
 - \land, \lor, \neg operate on truth/falsity of claims
 - Just as and, or and not combine statements
 - The way they operate give rise to certain laws
 - These laws provide rules for correct reasoning

マロト イヨト イヨト

Boolean Logic

The Boolean Connectives and Laws of Thought

Negation (\neg) : *Not*

A	¬A
TRUE	FALSE
FALSE	TRUE

Conjunction (\land): And

А	В	$A \wedge B$
TRUE	TRUE	TRUE
TRUE	FALSE	FALSE
FALSE	TRUE	FALSE
FALSE	FALSE	FALSE

Disjunction (\lor): Or

А	В	$A \lor B$
TRUE	TRUE	TRUE
TRUE	FALSE	TRUE
FALSE	TRUE	TRUE
FALSE	FALSE	FALSE

- ▶ ¬ flips truth/falsity
- \blacktriangleright \land takes worstvalue
- V takes bestvalue

Shannon's Insight

Electrical Boolean Circuits



- 1. Boole's variables become switches
- 2. Truth becomes current flowing (closed)
- 3. Falsity becomes current not flowing (open)

Shannon's Insight

Electrical Boolean Circuits



- 1. Boole's variables become switches
- 2. Truth becomes current flowing (closed)
- 3. Falsity becomes current not flowing (open)

Shannon's Insight

Mechanical OR Circuit



・ロン ・回 と ・ ヨン ・ ヨン

æ

Shannon's Insight

Isn't Specific to Electricity: Hydraulic OR



What is a Bit? A Binary Sigal

What's Common?

v combines truth-values (True/False)

(4回) (4回) (4回)

æ

What is a Bit? A Binary Sigal

What's Common?

- v combines truth-values (True/False)
- Electrical OR combines binary currents (High/Low)

< 🗇 > < 🖃 >

- ∢ ≣ >

What is a Bit? A Binary Sigal

- v combines truth-values (True/False)
- Electrical OR combines binary currents (High/Low)
- Mechanical OR combines binary stick positions (Moved Right/Not Moved Right)

What is a Bit? A Binary Sigal

- v combines truth-values (True/False)
- Electrical OR combines binary currents (High/Low)
- Mechanical OR combines binary stick positions (Moved Right/Not Moved Right)
- Hydraulic OR combines binary water pressures (Present/Absent)

What is a Bit? A Binary Sigal

- v combines truth-values (True/False)
- Electrical OR combines binary currents (High/Low)
- Mechanical OR combines binary stick positions (Moved Right/Not Moved Right)
- Hydraulic OR combines binary water pressures (Present/Absent)
- Abstraction: these are all binary signals!

What is a Bit? A Binary Sigal

- v combines truth-values (True/False)
- Electrical OR combines binary currents (High/Low)
- Mechanical OR combines binary stick positions (Moved Right/Not Moved Right)
- Hydraulic OR combines binary water pressures (Present/Absent)
- Abstraction: these are all binary signals!
- Definition: A bit is any binary signal

Thinking of Bits as 1's and 0's

Forget About The Details, Example of OR

Disjunction and Mechanical OR

A	В	$A \lor B$
TRUE	TRUE	TRUE
TRUE	FALSE	TRUE
FALSE	TRUE	TRUE
FALSE	FALSE	FALSE



A⊒ ▶ ∢ ∃

Thinking of Bits as 1's and 0's

Forget About The Details, Example of OR

Disjunction and Mechanical OR

A	В	$A \lor B$
TRUE	TRUE	TRUE
TRUE	FALSE	TRUE
FALSE	TRUE	TRUE
FALSE	FALSE	FALSE



0 Forget what 1 & 0 really are and how those things are combined!

OR in Bits B

N

A⊒ ▶ ∢ ∃

Α 1 1

1 0

0 0 A OR B

Logic Functions

- 1. A logic function is any way of taking in bits and responding with bits
- 2. Any way of taking in 1's and 0's and responding with 1's and 0's $% \left(1^{2}\right) =0$

Logic Functions

- 1. A logic function is any way of taking in bits and responding with bits
- 2. Any way of taking in 1's and 0's and responding with 1's and 0's $% \left(1^{2}\right) =0$
- Carrying out a logic function: crunching bits

Logic Functions

- 1. A logic function is any way of taking in bits and responding with bits
- 2. Any way of taking in 1's and 0's and responding with 1's and 0's $% \left(1^{2}\right) =0$
- Carrying out a logic function: *crunching bits* Bit Crunchers (Logic Functions) So Far
 - 1. AND
 - 2. OR
 - 3. INVERT

Bit Crunchers (Logic Functions) So Far

- 1. AND
- 2. OR
- 3. INVERT

Questions about Bit Crunching

1. Are there any bit crunching tasks these three can't do?

Bit Crunchers (Logic Functions) So Far

- 1. AND
- 2. OR
- 3. INVERT

Questions about Bit Crunching

- 1. Are there any bit crunching tasks these three can't do?
- 2. These just take in 2 bits and spit out 1, how do we do tasks involving more inputs and outputs?

Bit Crunchers (Logic Functions) So Far

- 1. AND
- 2. OR
- 3. INVERT

Questions about Bit Crunching

- 1. Are there any bit crunching tasks these three can't do?
- 2. These just take in 2 bits and spit out 1, how do we do tasks involving more inputs and outputs?
- 3. Why do we care about either of the questions above?

Answering the First Question

The Nature of Bit Crunching

Question 1

Are there any bit crunching tasks which (together) AND, OR and INVERT can't perform?

Answer

 No: together AND, OR and INVERT can perform any logic function

Answering the First Question

The Nature of Bit Crunching

Question 1

Are there any bit crunching tasks which (together) AND, OR and INVERT can't perform?

Answer

- No: together AND, OR and INVERT can perform any logic function
- In fact: just OR + INVERT or AND + INVERT can perform any logic function

Answering the First Question

The Nature of Bit Crunching

Question 1

Are there any bit crunching tasks which (together) AND, OR and INVERT can't perform?

Answer

- No: together AND, OR and INVERT can perform any logic function
- In fact: just OR + INVERT or AND + INVERT can perform any logic function
- Recall from last class that INVERT and OR can be combined to do what AND does

Answering the Second Question

More on the Nature of Bit Crunching

Question 2

AND, OR and INVERT just take in 2 bits and spit out 1, how do we do tasks involving more inputs and outputs?

Answering the Second Question

More on the Nature of Bit Crunching

Question 2

AND, OR and INVERT just take in 2 bits and spit out 1, how do we do tasks involving more inputs and outputs?

Answer

 By chaining together AND, OR and INVERT one can construct bit crunchers that take in more than 2 bits and spit out more than 1

Three Inputs By Combining ORs



FIGURE 10

A three-input Or block made from a pair of two-input Or blocks

Majority Rules

Take-in 3, Put-out 1

	Majority
Inputs	Output
ABC	
000	0
001	0
010	0
011	1
100	0
101	1
1 1 0	1
1 1 1	1

・ロン ・四と ・ヨン ・ヨン

æ

Majority Rules Diagram, v1

Take-in 3, Put-out 1



Majority Rules Diagram, v2 Take-in 3, Put-out 1



æ

Answering Question 3

Why You Should Care about the Nature of Bit Crunchers

Question 3

Why care whether Boolean circuits can do any bit crunching task? Why care about more than 2 inputs or more than 1 output?

Answer

 Now we know that any bit crunching task can be reduced to two incredibly simple tasks

Answering Question 3

Why You Should Care about the Nature of Bit Crunchers

Question 3

Why care whether Boolean circuits can do any bit crunching task? Why care about more than 2 inputs or more than 1 output?

Answer

- Now we know that any bit crunching task can be reduced to two incredibly simple tasks
 - So by studying these bit crunchers, we can figure out what any bit crunchers could do
Answering Question 3

Why You Should Care about the Nature of Bit Crunchers

Question 3

Why care whether Boolean circuits can do any bit crunching task? Why care about more than 2 inputs or more than 1 output?

Answer

- Now we know that any bit crunching task can be reduced to two incredibly simple tasks
 - So by studying these bit crunchers, we can figure out what *any* bit crunchers could do
- Minds do things that require >2 inputs and outputs

Answering Question 3

Why You Should Care about the Nature of Bit Crunchers

Question 3

Why care whether Boolean circuits can do any bit crunching task? Why care about more than 2 inputs or more than 1 output?

Answer

- Now we know that any bit crunching task can be reduced to two incredibly simple tasks
 - So by studying these bit crunchers, we can figure out what *any* bit crunchers could do
- Minds do things that require >2 inputs and outputs
 - E.g. judging the winner of Rock-Paper-Scissors

▲圖 ▶ ▲ 臣 ▶ ▲ 臣 ▶ …

Rock-Paper-Scissors Judge Ternary Input, Ternary Output!

Input A	Input B	Output	
Scissors	Scissors	Tie	
Scissors	Paper	A wins	
Scissors	Rock	B wins	
Paper	Scissors	B wins	
Paper	Paper	Tie	
Paper	Rock	A wins	
Rock	Scissors	A wins	
Rock	Paper	B wins	
Rock	Rock	Tie	

Image: A = A = A

- < ≣ →

æ

Rock-Paper-Scissors

Using Two Binary Inputs to Mimic One Ternary Input

	A Inputs	B Inputs	Outputs
	01	01	00
	01	10	10
Scissors = 01	01	11	01
Paper = 10	10	01	01
Rock = 11	10	10	00
A wins = 10	10	11	10
B wins = 01	11	01	10
Tie = 00	11	10	01
	11	11	00

| 4 回 2 4 U = 2 4 U =

æ

Bit Crunching

The Core Idea

What is a Bit Cruncher?

Takes x input bits and returns y output bits

<**□** > < ⊇ >

_∢ ≣ ≯

Bit Crunching

The Core Idea

What is a Bit Cruncher?

Takes x input bits and returns y output bits

For each set of x inputs, there is a set of y outputs that is always the result of that input

Bit Crunching

The Core Idea

What is a Bit Cruncher?

- For each set of x inputs, there is a set of y outputs that is always the result of that input
- Constant behavior with respect to inputs

Bit Crunching

The Core Idea

What is a Bit Cruncher?

- For each set of x inputs, there is a set of y outputs that is always the result of that input
- Constant behavior with respect to inputs
- Input 1 to a NOT circuit; you always get a 0 back!

Bit Crunching

The Core Idea

What is a Bit Cruncher?

- For each set of x inputs, there is a set of y outputs that is always the result of that input
- Constant behavior with respect to inputs
- Input 1 to a NOT circuit; you always get a 0 back!
- Thinking of inputs as perceptions, does this seem like an adequate account of minds?

Bit Crunching

The Core Idea

What is a Bit Cruncher?

- For each set of x inputs, there is a set of y outputs that is always the result of that input
- Constant behavior with respect to inputs
- Input 1 to a NOT circuit; you always get a 0 back!
- Thinking of inputs as perceptions, does this seem like an adequate account of minds?
- Are minds just giant Boolean circuits? ('Logic blocks')

Outline

What Can a Boolean Circuit Do?

Finite State Machines

・ロン ・回 と ・ ヨン ・ ヨン

æ

You Don't Always Do the Same Thing in Response to a Signal

Logic blocks always react to the same signal/input in the same way, but things with minds don't!

・ 同 ト ・ ヨ ト ・ ヨ ト

- Logic blocks always react to the same signal/input in the same way, but things with minds don't!
- Minds react on the basis of their previous experiences!

- Logic blocks always react to the same signal/input in the same way, but things with minds don't!
- Minds react on the basis of their previous experiences!
- Even very simple machines do this:

- Logic blocks always react to the same signal/input in the same way, but things with minds don't!
- Minds react on the basis of their previous experiences!
- Even very simple machines do this:
 - Clicking pen, combo lock

- Logic blocks always react to the same signal/input in the same way, but things with minds don't!
- Minds react on the basis of their previous experiences!
- Even very simple machines do this:
 - Clicking pen, combo lock
- Machines which monitor and change an internal register: Finite State Machines

- Logic blocks always react to the same signal/input in the same way, but things with minds don't!
- Minds react on the basis of their previous experiences!
- Even very simple machines do this:
 - Clicking pen, combo lock
- Machines which monitor and change an internal register: Finite State Machines
 - 'Register': a limited, finite memory

- Logic blocks always react to the same signal/input in the same way, but things with minds don't!
- Minds react on the basis of their previous experiences!
- Even very simple machines do this:
 - Clicking pen, combo lock
- Machines which monitor and change an internal register: Finite State Machines
 - 'Register': a limited, finite memory
- Register keeps track of the previous input

You Don't Always Do the Same Thing in Response to a Signal

- Logic blocks always react to the same signal/input in the same way, but things with minds don't!
- Minds react on the basis of their previous experiences!
- Even very simple machines do this:
 - Clicking pen, combo lock
- Machines which monitor and change an internal register: Finite State Machines
 - 'Register': a limited, finite memory
- Register keeps track of the previous input
- Register is itself is a Boolean circuit

・ 同 ト ・ 三 ト ・ 三 ト

Combo Lock For 0-5-2 (p.36)



Combo Lock For 0-5-2 (p.36)



Combo Lock For 0-5-2 (p.36)



Combo Lock For 0-5-2 (p.36)



FSMs Listen to Themselves

What is Computation?

Response = input + current state

æ

Current state = previous input

Stoplight Controller

As a Finite State Machine



イロト イヨト イヨト イヨト

æ

How A Stoplight Works

In Terms of Input/Output

Inputs:	puts: Outputs:			
Walk	Current	Main	Cross	Next
Button	State	Road	Road	State
Not Pressed	А	Red	Green	В
Not Pressed	В	Red	Yellow	D
Not Pressed	С	Yellow	Red	Α
Not Pressed	D	Green	Red	С
Not Pressed	Walk	Walk	Walk	D
Pressed	Α	Red	Green	В
Pressed	В	Red	Yellow	Walk
Pressed	С	Yellow	Red	Walk
Pressed	D	Green	Red	С
Pressed	Walk	Walk	Walk	Walk

イロン イヨン イヨン イヨン

æ

Finite State Machines

The Mealy Machine



FIGURE 14

Finite-state machine, with logic block feeding register

(G.H. Mealy, "A Method for Synthesizing Sequential Circuits" 1955) 💿 👁

Carlotta Pavese What is Computation?

In General

In General

1. Register built from Boolean circuits

(4回) (4回) (4回)

æ

In General

- 1. Register built from Boolean circuits
- 2. Register and inputs feed into second logic block

In General

- 1. Register built from Boolean circuits
- 2. Register and inputs feed into second logic block
- 3. This logic block produces an output and sends bits back to register

In General

- 1. Register built from Boolean circuits
- 2. Register and inputs feed into second logic block
- 3. This logic block produces an output and sends bits back to register
- 4. Register crunches these bits

In General

- 1. Register built from Boolean circuits
- 2. Register and inputs feed into second logic block
- 3. This logic block produces an output and sends bits back to register
- 4. Register crunches these bits
- 5. And then the cycle repeats

In General

- 1. Register built from Boolean circuits
- 2. Register and inputs feed into second logic block
- 3. This logic block produces an output and sends bits back to register
- 4. Register crunches these bits
- 5. And then the cycle repeats
- This allows finite state machines to recognize patterns

In General

- 1. Register built from Boolean circuits
- 2. Register and inputs feed into second logic block
- 3. This logic block produces an output and sends bits back to register
- 4. Register crunches these bits
- 5. And then the cycle repeats
- This allows finite state machines to recognize patterns
- All patterns?

Recognizing Patterns: begins w/1, any number of 0s, ends w/3 (p.35)



æ

Recognizing Patterns: begins w/1, any number of 0s, ends w/3 (p.35)



Important

There is one state for each digit that has to be remembered.

Recognizing Patterns

Palindrome

A string of symbols which is the same whether read backwards or forwards.

• E.g. 99, 757, 1001, abba, abccba, dad, mom
Recognizing Patterns

Palindrome

A string of symbols which is the same whether read backwards or forwards.

- ► E.g. 99, 757, 1001, abba, abccba, dad, mom
- A finite state combo lock that detects only palindromes is not possible (even if alphabet is finite)

Recognizing Patterns

Palindrome

A string of symbols which is the same whether read backwards or forwards.

- E.g. 99, 757, 1001, abba, abccba, dad, mom
- A finite state combo lock that detects only palindromes is not possible (even if alphabet is finite)

Why

To recognize a palindrome, you need to remember every digit of the first half. You need one state for each such memory. But there are infinitely many first halves, so you would need infinitely many states.

And Human Language

 Chomsky (Syntactic Structures 1957) argued an FSM could not recognize all sentences of a human language

- Chomsky (Syntactic Structures 1957) argued an FSM could not recognize all sentences of a human language
- Consider a sentence of this form:

- Chomsky (Syntactic Structures 1957) argued an FSM could not recognize all sentences of a human language
- Consider a sentence of this form:
 - Either S₁ or S₂
 (S₁ and S₂ are sentences)

- Chomsky (Syntactic Structures 1957) argued an FSM could not recognize all sentences of a human language
- Consider a sentence of this form:
 - Either S₁ or S₂
 (S₁ and S₂ are sentences)
 - E.g. Either Jill is happy or Sarah is happy

- Chomsky (Syntactic Structures 1957) argued an FSM could not recognize all sentences of a human language
- Consider a sentence of this form:
 - Either S_1 or S_2
 - $(S_1 \text{ and } S_2 \text{ are sentences})$
 - E.g. Either Jill is happy or Sarah is happy
- ► To recognize all sentences of this form, a FSM would have to have a state for each different S₁

- Chomsky (Syntactic Structures 1957) argued an FSM could not recognize all sentences of a human language
- Consider a sentence of this form:
 - Either S_1 or S_2
 - $(S_1 \text{ and } S_2 \text{ are sentences})$
 - E.g. Either Jill is happy or Sarah is happy
- ► To recognize all sentences of this form, a FSM would have to have a state for each different S₁
- But there are infinitely many!

- Chomsky (Syntactic Structures 1957) argued an FSM could not recognize all sentences of a human language
- Consider a sentence of this form:
 - Either S_1 or S_2
 - $(S_1 \text{ and } S_2 \text{ are sentences})$
 - E.g. Either Jill is happy or Sarah is happy
- ► To recognize all sentences of this form, a FSM would have to have a state for each different S₁
- But there are infinitely many!
- Think you've found the last sentence? Call it S.

And Human Language

- Chomsky (Syntactic Structures 1957) argued an FSM could not recognize all sentences of a human language
- Consider a sentence of this form:
 - Either S_1 or S_2
 - $(S_1 \text{ and } S_2 \text{ are sentences})$
 - E.g. Either Jill is happy or Sarah is happy
- ► To recognize all sentences of this form, a FSM would have to have a state for each different S₁
- But there are infinitely many!
- ► Think you've found the last sentence? Call it S.
- Isn't this a sentence: I don't believe that S?

- < ≣ > -

What Can a Boolean Circuit Do? Finite State Machines

Reading For 10.22

Required Ch. 3 of *The Pattern on the Stone* Recommended

Carlotta Pavese What is Computation?

< 4 → < 2

< ≣⇒

æ